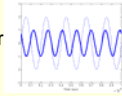


ECE 2704
Signals and Systems
Spring 2006

Instructor: Dr. R. Michael Buehrer
Lecture #16: Applications of the Fourier
Transform – Part II: Practical Filters
and Bode Diagrams



Overview




- Today we continue our discussion of applications of the Continuous Time Fourier Transform (CTFT)
- We specifically consider
 - Practical Filters
 - Bode plots
 - Log-magnitude plots
 - Communication example
- What to read – Sections 6.4-6.5, 6.9 in the text


Resistors, capacitors, inductors



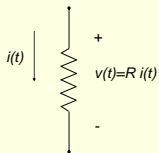
- The voltage across an element in a circuit can be written as



Resistor

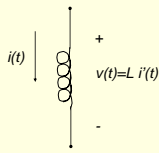

Inductor

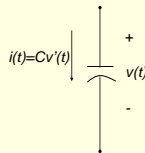

Capacitor

Frequency Domain



- Using our knowledge of Fourier Transforms, we can write the relationship between voltage and current for each:

Resistor

$$\frac{V(f)}{I(f)} = R$$

Inductor

$$\frac{V(f)}{I(f)} = j2\pi fL$$

Capacitor

$$\frac{V(f)}{I(f)} = \frac{1}{j2\pi fC}$$

- Using radian frequency $\omega = 2\pi f$

$$\frac{V(j\omega)}{I(j\omega)} = R$$

$$\frac{V(j\omega)}{I(j\omega)} = j\omega L$$

$$\frac{V(j\omega)}{I(j\omega)} = \frac{1}{j\omega C}$$

- This gives rise to the concept of *impedance* $Z(\omega)$


$$Z(j\omega) = \frac{V(j\omega)}{I(j\omega)} \quad Z(f) = \frac{V(f)}{I(f)}$$

Signals & Systems
Spring 2006
R. M. Mersereau

RC Lowpass Filter



- Consider an RC circuit of the form

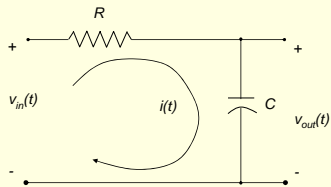

- Using Kirchoff's Voltage law

$$v_{in}(t) = i(t)R + v_{out}(t)$$

$$= v'_{out}(t)RC + v_{out}(t)$$

Signals & Systems
Spring 2006
R. M. Mersereau

RC Filter (cont.)



- We could solve this using differential equations as we did in the past. However, using Fourier Transforms is more straightforward.

$$v_{in}(t) = v'_{out}(t)RC + v_{out}(t)$$

- Taking the Fourier Transform of both sides

$$V_{in}(f) = j2\pi f V_{out}(f)RC + V_{out}(f)$$

- Now we can directly solve for the system transfer function

$$H(f) = \frac{V_{out}(f)}{V_{in}(f)}$$

$$= \frac{1}{1 + j2\pi fRC}$$

Signals & Systems
Spring 2006
R. M. Mersereau

RC Filter – cont.

- The system transfer function can be plotted in terms of its magnitude response and phase response

$$H(f) = \frac{1}{1 + j2\pi fRC}$$


$$|H(f)| = \frac{1}{\sqrt{1 + (2\pi fRC)^2}}$$

$$\begin{aligned} \angle H(f) &= 0 - \tan^{-1}(2\pi fRC) \\ &= -\tan^{-1}(2\pi fRC) \end{aligned}$$


Signals & Systems
Spring 2006
Rabbani

RC Filter – Magnitude and Phase

Magnitude Response

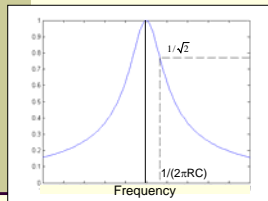

Phase Response

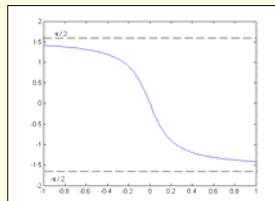


Clearly this is a low pass filter with a 3dB bandwidth of $1/(2\pi RC)$. However, note that it is defined as lowpass strictly because of the input and output definitions

Signals & Systems
Spring 2006
Rabbani

RLC Bandpass Filter

- Consider the following circuit

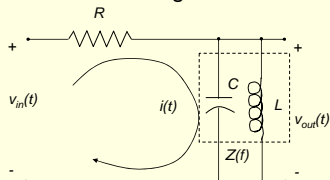

- If we define the combined capacitor and inductor to have an impedance $Z(f)$, we can solve the problem just as in the previous case
- We will use the frequency domain directly

Signals & Systems
Spring 2006
Rabbani

Single Pole Filter



- Consider a filter with system transfer function

$$H(f) = \frac{1}{1 + j2\pi f / p_1}$$

- At very low and high frequencies we have

$$H(f) \approx 1 \quad 2\pi f \ll p_1$$

$$H(f) \approx \frac{p_1}{j2\pi f} \quad 2\pi f \gg p_1$$

- Thus, at low frequencies, the filter response is unity and at high frequencies the filter response is inversely proportional with $2\pi f$

Single Pole Filter – cont.



- Consider two high frequencies f_1 and $f_2 = 10f_1$

$$20 \log_{10} |H(f_1)| \approx 20 \log_{10} \left(\frac{p_1}{2\pi f_1} \right)$$

$$20 \log_{10} |H(f_2)| \approx 20 \log_{10} \left(\frac{p_1}{2\pi f_2} \right)$$

$$= 20 \log_{10} \left(\frac{p_1}{2\pi 10 f_1} \right)$$

$$= 20 \log_{10} \left(\frac{1}{10} \right) + 20 \log_{10} \left(\frac{p_1}{2\pi f_1} \right)$$

$$= 20 \log_{10} \left(\frac{p_1}{2\pi f_1} \right) - 20 \text{dB}$$


- A change in frequency of a factor of ten is termed a *decade*.
- A change in frequency by a factor of two is termed an *octave*
- Thus, a single pole filter response decays at 20dB per decade or 6dB per octave

Single Pole Filter – cont.




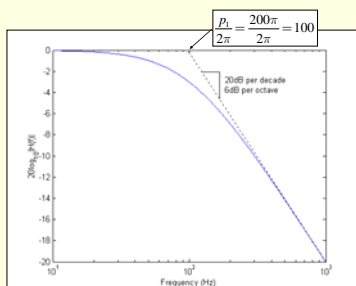
- Example

$$H(f) = \frac{1}{1 + j2\pi f / (200\pi)}$$



AM – cont.

- Zooming in...

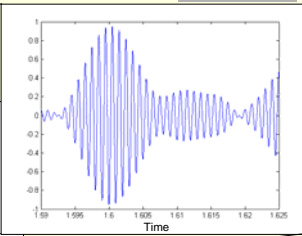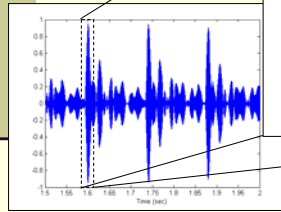


Carrier has amplitude that is varying according to the message

Signals & Systems
Spring 2006
Rudolf

AM – cont.

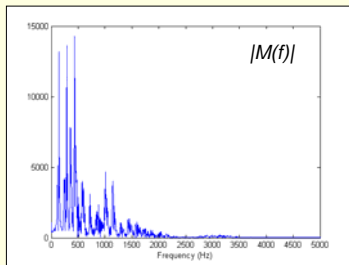- Message Signal Spectrum
- Voice signal has most of its energy below 4kHz




Signals & Systems
Spring 2006
Rudolf

AM - cont.

- After modulation the spectrum of the signal is centered at the carrier frequency (20kHz in this example)
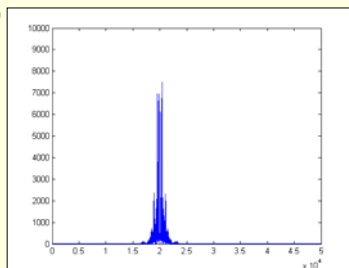
$$X(f) = \frac{1}{2} \{M(f - f_c) + M(f + f_c)\}$$



Signals & Systems
Spring 2006
Rudolf


AM – cont.



- An AM radio must select one signal from several received signals.
- We can visualize what the receiver must do by examining the frequency domain:



If we desire to listen to channel 2, the receiver must use a bandpass filter to isolate the second signal from the others

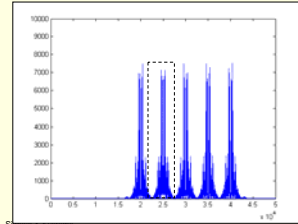This would be extremely hard to visualize in the time domain



Signals & Systems
Spring 2006
Rudolf

AM – cont.

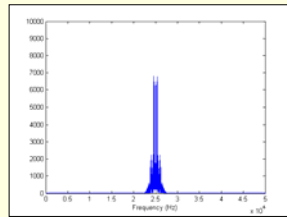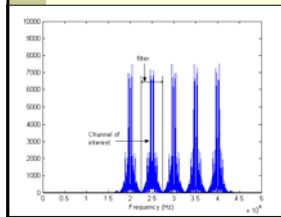

Signals & Systems
Spring 2006
Rudolf

Summary



- In this lecture we have examined further application of the Fourier Transform
- Specifically we have looked at the practical lowpass and bandpass filters using simple RLC circuits.
- We also showed how these circuits are analyzed through the use of Bode plots and component diagrams
- We finished with a common but simple communications example – AM modulation

Signals & Systems
Spring 2006
Rudolf
